NESVERTER

Up Up Up

Just add more solder !

MICROMEET – 2026

L. Cupido - CT1DMK

“Is better to know useless things then to know nothing” Seneca

Going up in frequency *(or life becomes boring)*

24GHz, 47GHz 76GHz etc…

Whatever you do higher frequency LO is desirable.

Low cost ADF4351 synthesizer boards go to about 4.4 GHz

- a doubler takes 2.6 into 5.2GHz, for a 10GHz Nesverter, **Done ✔**

- a tripler will take 3.8 into 11.4GHz, for a 24GHz Nesverter

So… **Lets make a Tripler !!!!**

Tripler, diagram:

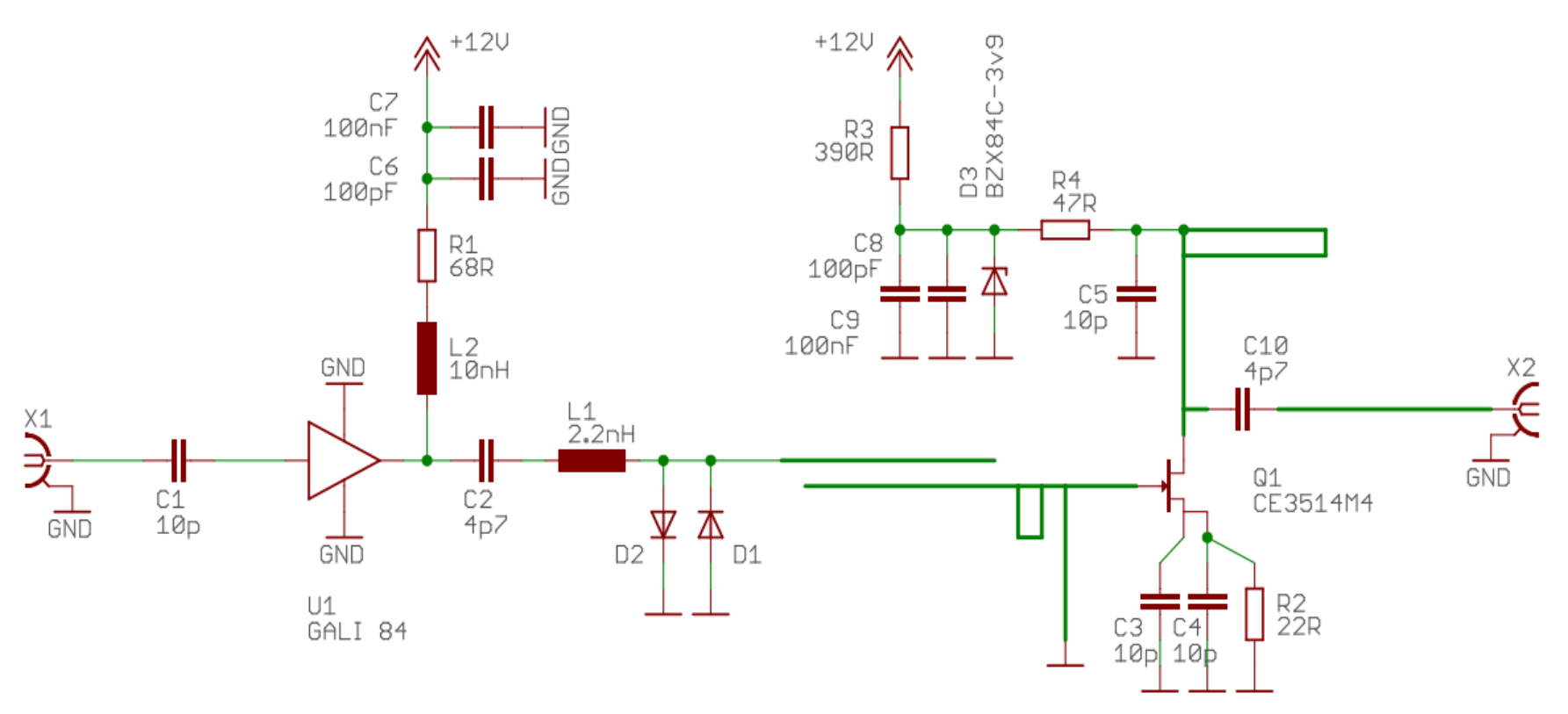

Yet another instant prototype:

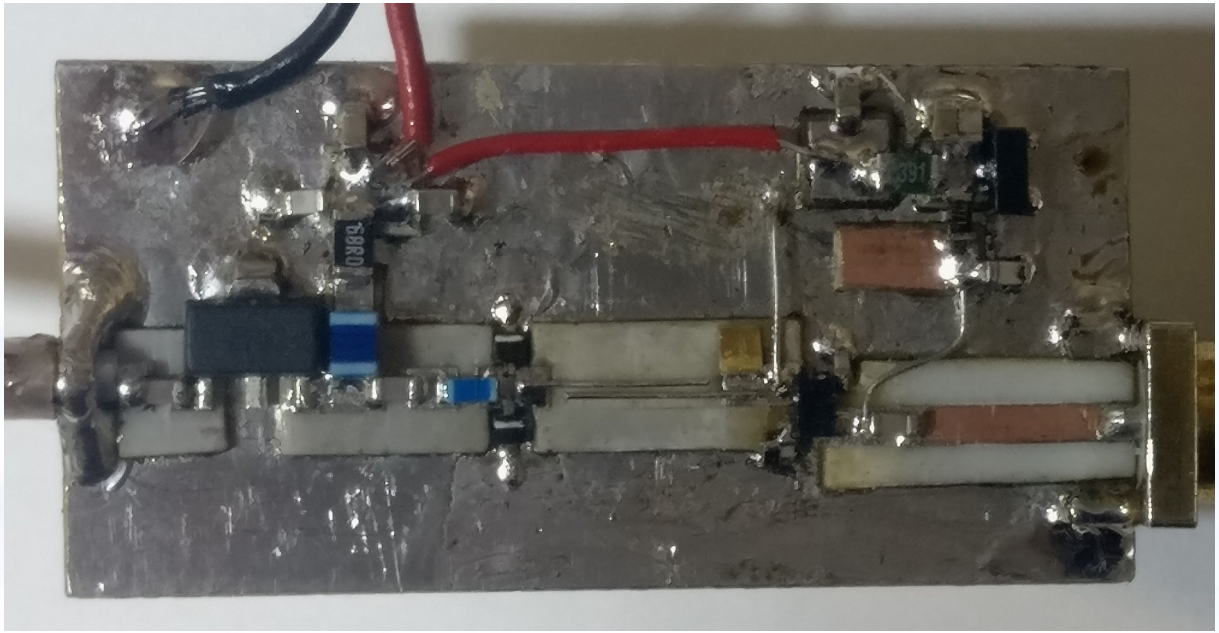

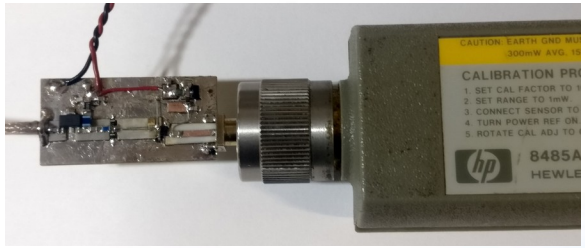

Gracias

Obrigado

Thanks